

C13-R3: DIGITAL SYSTEM DESIGN

NOTE:

1. Answer question 1 and any FOUR from questions 2 to 7.
2. Parts of the same question should be answered together and in the same sequence.

Time: 3 Hours

Total Marks: 100

1.

- a) Compare f_{\max} of a 4-bit ripple counter with that of a 4-bit synchronous counter using J-K FFs. The t_{pd} for each FF is 50ns and t_{pd} for each AND gate is 20ns. What needs to be done to convert these counters to mod-32? Determine f_{\max} for the mod-32 ripple and parallel counters.
- b) Derive a truth table for the following expression (F) by showing each element in the truth table and minimize the function (F).

$$F = \overline{A} \cdot \overline{C} \cdot (B \oplus D) + A \cdot \overline{C} \cdot \overline{(B \oplus \overline{D})} + B \cdot \overline{C} \cdot D + \overline{B + C + D}$$

- c) Convert a clocked D flipflop to a clocked JK flipflop by adding external gates.
- d) Find the base of the following operation:
 $23+44+14+32=223$
- e) VHDL is a concurrent language. Show its use in the design of sequential circuit.
- f) Differentiate between inertial delay model and Transport delay model in terms of signal assignments.
- g) Explain threshold voltage and Noise margin for CMOS inverter.

(7x4)

2.

- a) Realize $F_1(a,b,c)=\sum m(0,2,3,4,5)$, $F_2(a,b,c)=\sum m(0,2,3,4,7)$, $F_3(a,b,c)=\sum m(1,2,6,7)$ using only 2-input NAND gates.
- b) A sequential network contains a register of four flipflops. Initially a binary Number N ($0000 \leq N \leq 1001$) is stored in the flipflops. After a single input pulse is applied to the network, the register should contain $N+0101$. In other words, the function of the sequential network is to add 5 to the contents of a 4-bit register. Design the network using J-K flipflops.
- c) Design a sequence generator by using JK flipflops which goes through following sequences: 0,3,5,6 and repeat. Determine whether the counter is self starting or not?

(6+6+6)

3.

- a) Simplify the function using Karnaugh Graph $f(a, b, c, d) = \sum m(0, 2, 10, 11, 12, 14)$.
- b) Realize the following functions using a PLA. Show all steps of design.
 $F_1 = \sum m(2,3,5,7,8,9,10,11,13,15)$
 $F_2 = \sum m(2,3,5,6,7,10,11,14,15)$
 $F_3 = \sum m(6,7,8,9,13,14,15)$

(6+12)

4.

- a) Give VHDL description of a T flipflop.
- b) Using developed description of the T flipflop design a 3 bit asynchronous counter. Give VHDL description of a counter in a structural modeling style.

(9+9)

5.

- a) Draw a block diagram of a 4 bit serial adder with Accumulator. Explain operation of it and also describe control state graph.
- b) Explain static '1' hazard in combinational circuit by taking a suitable example.
- c) Using two 2-to-1 multiplexers (with no added gates) design a 3-to-1 multiplexer. Input selection should be as follows:

Input Selection	AB
I ₀	00
I ₁	01
I ₂	1X

(10+4+4)

6.

- a) Design a 2-input 2-output synchronous sequential circuit which produces an output z=1, whenever any of the following input sequences 1100, 1010 or 1001 occurs. The circuit resets to its initial state after a 1 output has been generated.
- b) Realize a 2-bit comparator to compare two 2-bit numbers, using appropriate demultiplexer with active high outputs and additional logic gates.
- c) Design a hexadecimal to binary encoder using 74148 encoders and 74157 multiplexer.

(6+6+6)

7.

- a) 4 unsigned 4-bit numbers are stored in a set of registers. Design a circuit that can sort the list in ascending order. Draw a possible system architecture diagram, showing different components, which are required for the design.
- b) Draw and explain the basic structure of FPGA. Explain functioning of logic cell using lookup table approach.
- c) Design the sequential circuit whose state table is given below using a 2-bit register and combinational gates.

Present State		Input X	Next state	
A	B		A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	0
1	1	1	0	1

(8+6+4)